

Problem 1

In Fig. 1 is shown an RLC circuit with a DC voltage source.

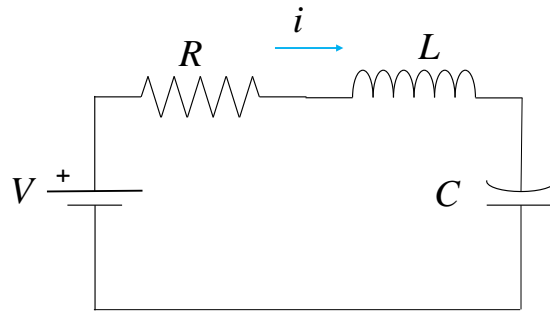


Figure 1 Electric circuit consisting of a DC voltage source, a resistor, an inductance and a capacitance.


The following data is given for the circuit: $R = 20 \, \Omega$, $L = 4 \, H$ and $C = 2.5 \, mF$.

The DC voltage source is ramped up from 0 V to 12 V in 0.5 seconds.

Initially there is no current in the inductance and no voltage drop across the capacitance.

Simulate the system for a period of 3 seconds.

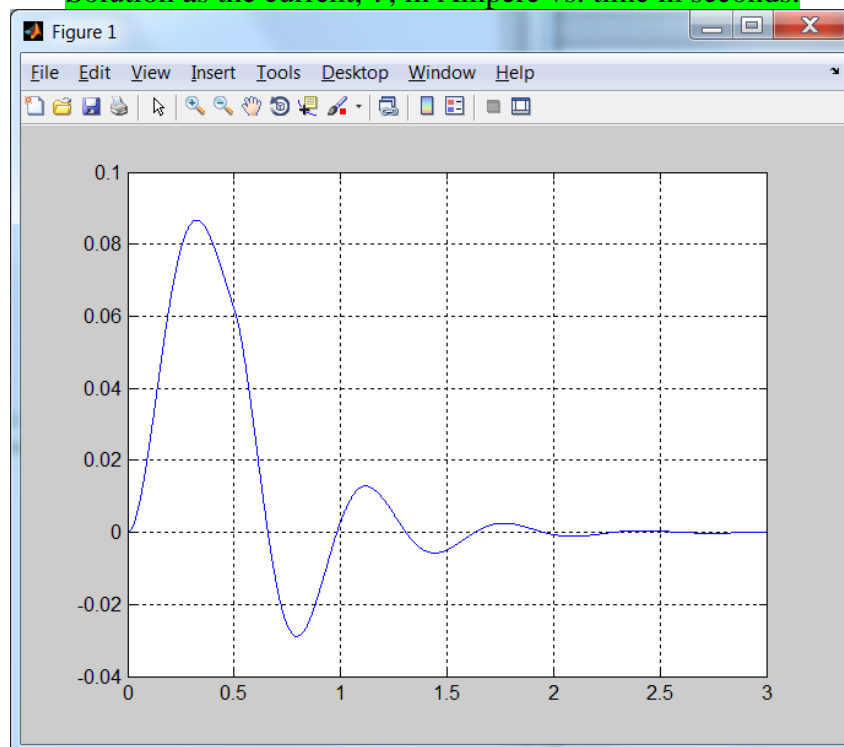Solution as the current, i , in Ampere vs. time in seconds.




The voltage source is replaced with an AC voltage source. The voltage amplitude of the AC voltage source is $\sqrt{2} \cdot V = 12V$ or RMS value of $V = 8.485V$ and the frequency may have three different values: $\omega = [5 \ 10 \ 15] \frac{rad}{s}$.


In the time domain this corresponds to a supply voltage of $V_s = \sqrt{2} \cdot V \cdot \sin(\omega \cdot t)$
Initially there is no current in the inductance and no voltage drop across the capacitance.

Simulate the system for a period of 5 seconds for all three different frequencies.

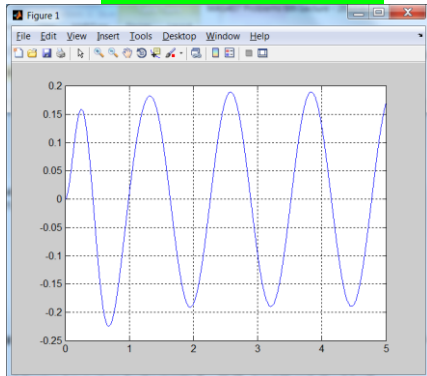
Solution as the current, i , in Ampere vs. time in seconds for $\omega = 5 \frac{rad}{s}$.



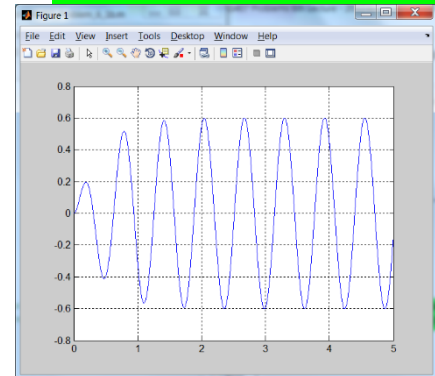Solution as the current, i , in Ampere vs. time in seconds for $\omega = 10 \frac{rad}{s}$.



Solution as the current, i , in Ampere vs. time in seconds $\omega = 15 \frac{rad}{s}$.

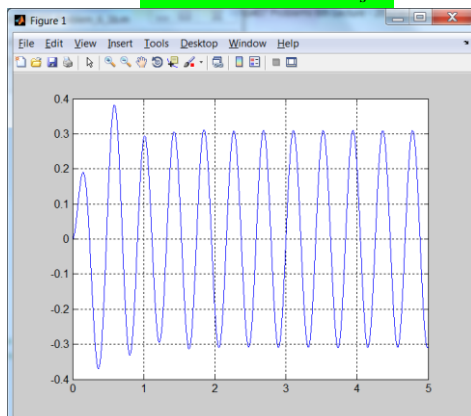

Problem 2

An electric circuit is shown in Fig. 2 and consists of a voltage supply, two resistors, and a capacitor. The two resistances have the same resistance $R_1 = R_2 = 200 \, \Omega$. The capacitance of the capacitor is $C = 60 \, \mu\text{F}$. The supply voltage is ramped up to a constant value of $U_S = 12 \, \text{V}$, according to Fig. 3.

At time $t = 0 \, \text{s}$ the voltage drop across the capacitor is $U_C = 24 \, \text{V}$.

Make a simulation model of the electric circuit in Matlab and plot the two currents i_1 and i_2 from $t = 0 \, \text{s}$ to $t = 0.5 \, \text{s}$. Also, plot the voltage drop across the capacitor.

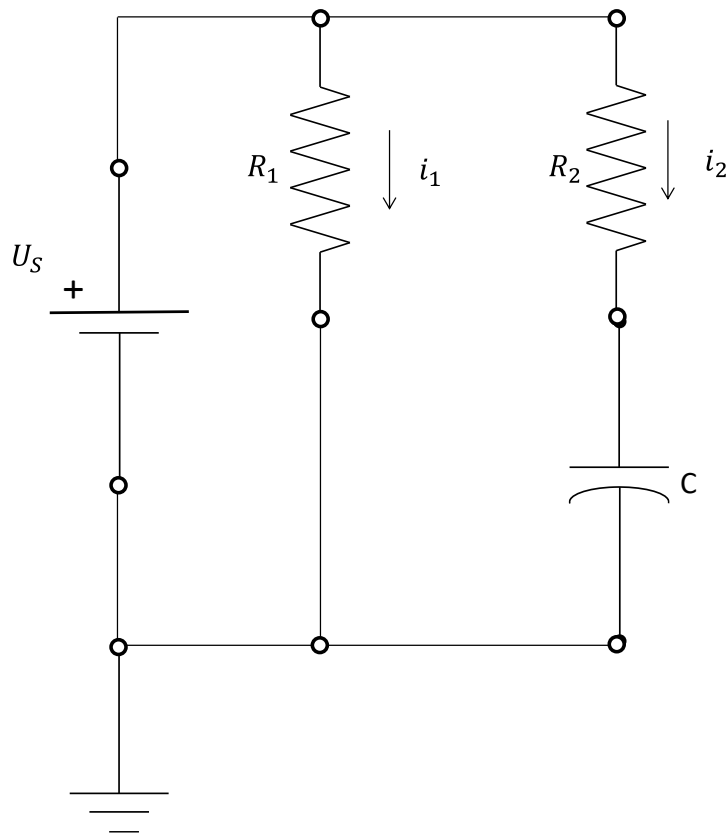


Figure 2 Electric circuit.



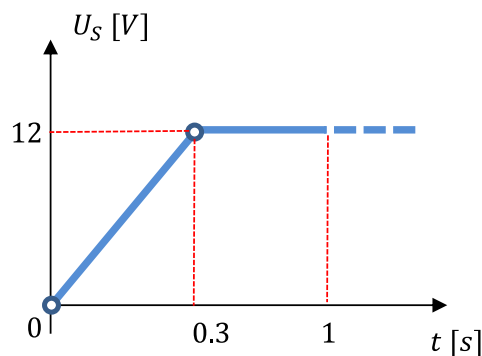


Figure 3 Variation of voltage supply vs. time.

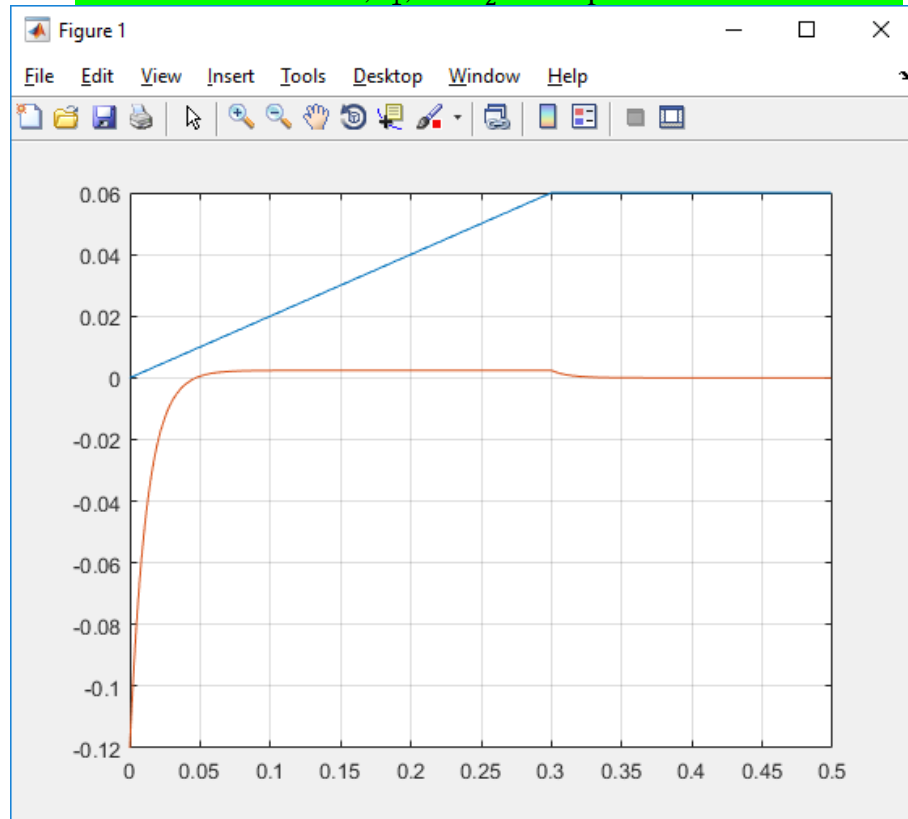Solution as the current, i_1 , and i_2 in Ampere vs. time in seconds.



Solution as the capacitor voltage drop, U_C , in Volt vs. time in seconds.

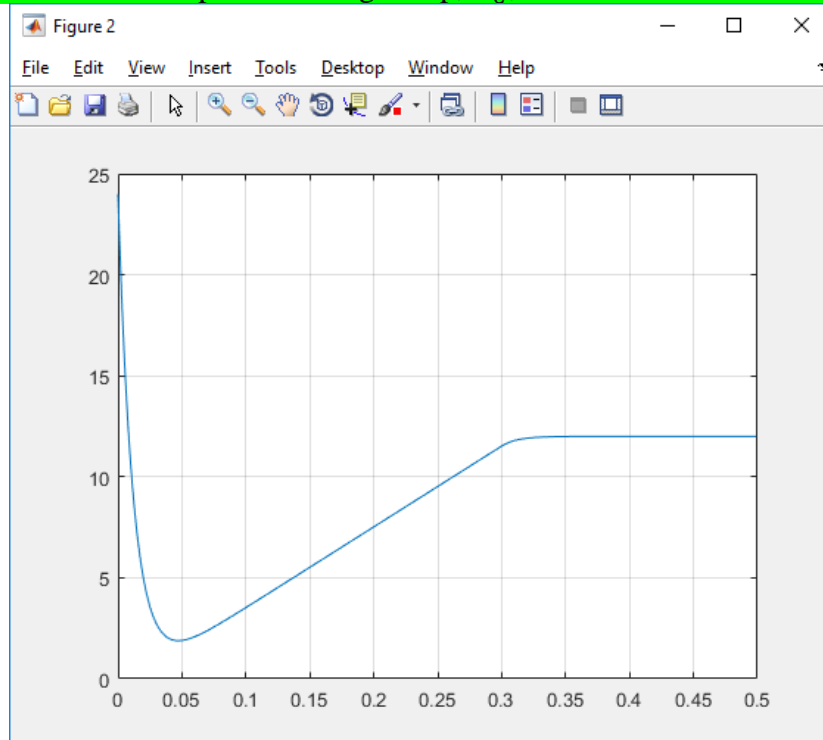

Problem 3


An electric circuit is shown in Fig. 3 and consists of an AC voltage source, a diode, a resistor, and a capacitor.

The resistance is $R_1 = 1500 \Omega$. The capacitance is $C_1 = 60 \mu\text{F}$. The RMS value of the voltage source is $V_1 = 120 \text{ V}$ and the frequency is $f_1 = 50 \text{ Hz}$.

The diode minimum resistance can be set to $R_{D1} = 1 \Omega$

At time $t = 0 \text{ s}$ the voltage drop across the capacitor is $U_C = 0 \text{ V}$.

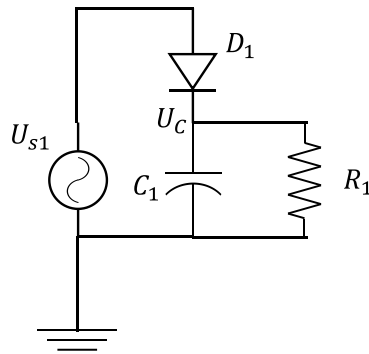
Make a simulation model of the electric circuit in Matlab and plot the capacitor voltage, U_C , and the supply voltage, U_{s1} , from $t = 0 \text{ s}$ to $t = 0.1 \text{ s}$.



$$U_{s1} = \sqrt{2} \cdot V_1 \cdot \sin(2 \cdot \pi \cdot f_1 \cdot t)$$

Figure 4: Electric circuit

Solution as the capacitor voltage drop, U_C , and the supply voltage, U_{s1} in Volt vs. time in seconds.

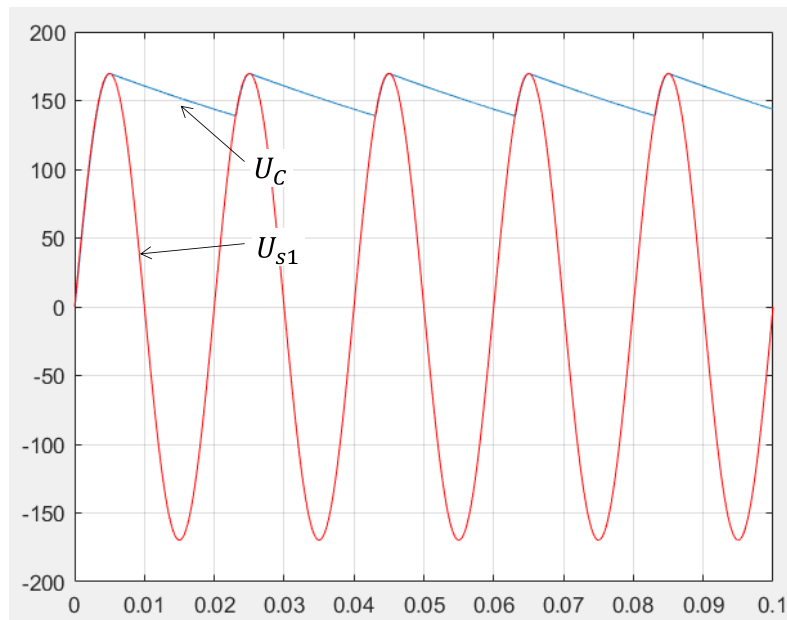

Problem 4

An electrical system is shown in Figure 5. It consists of two voltage supplies U_{S1} and U_{S2} , five resistances $R_{1..5}$, two capacitors $C_{1..2}$, and a single inductance L_1 .

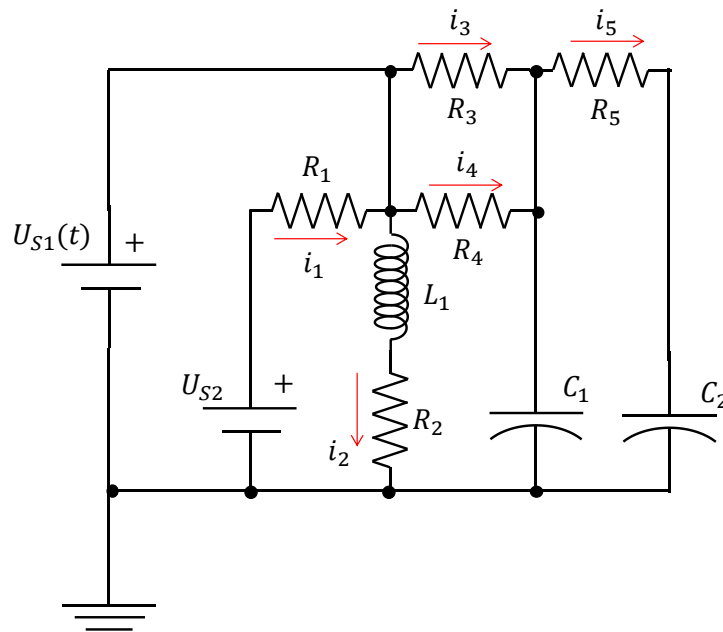


Figure 5 Electrical system.

The following data is given: $R_1 = 5000 \, \Omega$, $R_2 = 2000 \, \Omega$, $R_3 = R_5 = 1200 \, \Omega$, $R_4 = 8000 \, \Omega$, $C_1 = C_2 = 380 \, \mu F$, and $L_1 = 50 \, H$.

The first voltage supply is a function of time as shown in Figure 6:

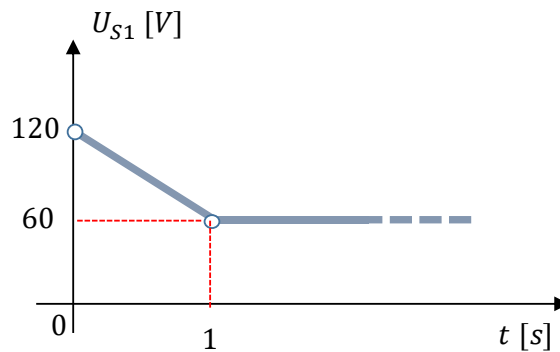



Figure 6 The voltage supply, U_{S1} , as a function of time.

The second voltage supply is constant at $U_{S2} = 120 \, V$.

At time $t = 0 \, s$ the voltage drops across the capacitances are $U_{C1} = U_{C2} = 60 \, V$ and the current through the inductance is $i_2 = 0 \, A$.

Make a simulation model of the electrical system and simulate from $t = 0 \, s$ to $t = 6 \, s$. Plot the currents $i_{1..5}$ as a function of time.

Solution as the current, i_1 (blue), i_2 (green), i_3 (cyan), i_4 (magenta), and i_5 (red) in mA vs. time in seconds.

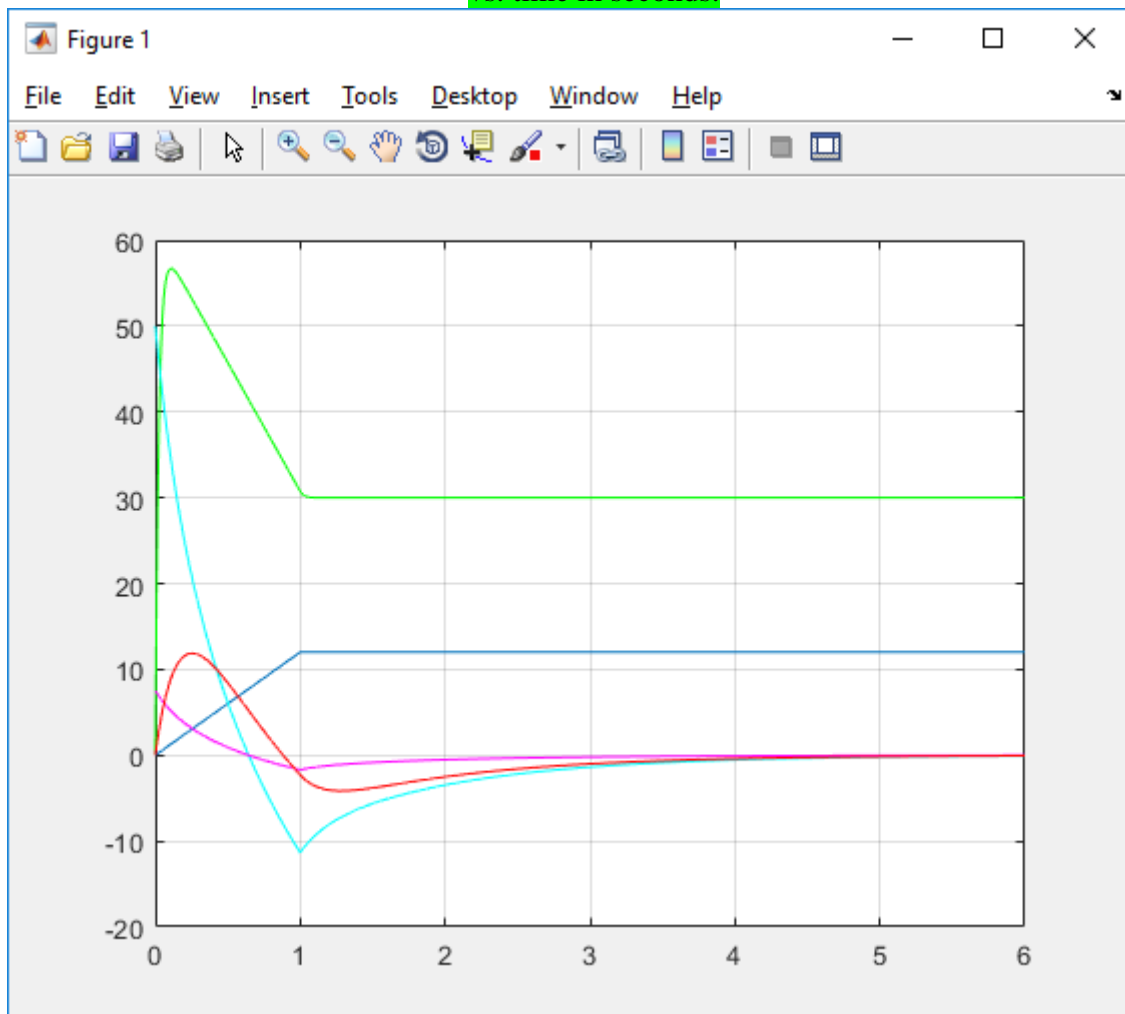

Problem 5

A DC motor is described by the following data: $J_m = J_{eff} = 2.5 \cdot 10^{-4} \text{ kg} \cdot \text{m}^2$, $V_a = 12 \text{ V}$, $R_a = 0.4 \Omega$, $L_a = 0.03 \text{ H}$, and $K_m = 0.1 \frac{\text{N} \cdot \text{m}}{\text{A}}$.


The load on the rotor is a friction torque given as: $M_L = M_{fr} \cdot \tanh\left(\frac{\omega_m}{\omega_{fr}}\right)$, where $M_{fr} = 0.2 \text{ N} \cdot \text{m}$

and $\omega_{fr} = 20 \frac{\text{rad}}{\text{s}}$.

Initially the rotor has no rotation and is at rest. Also, initially, there is no current in the armature inductance.

Simulate the system for a period of 2 seconds.

Solution as the motor speed, ω_m , in radians pr. second vs. time in seconds.

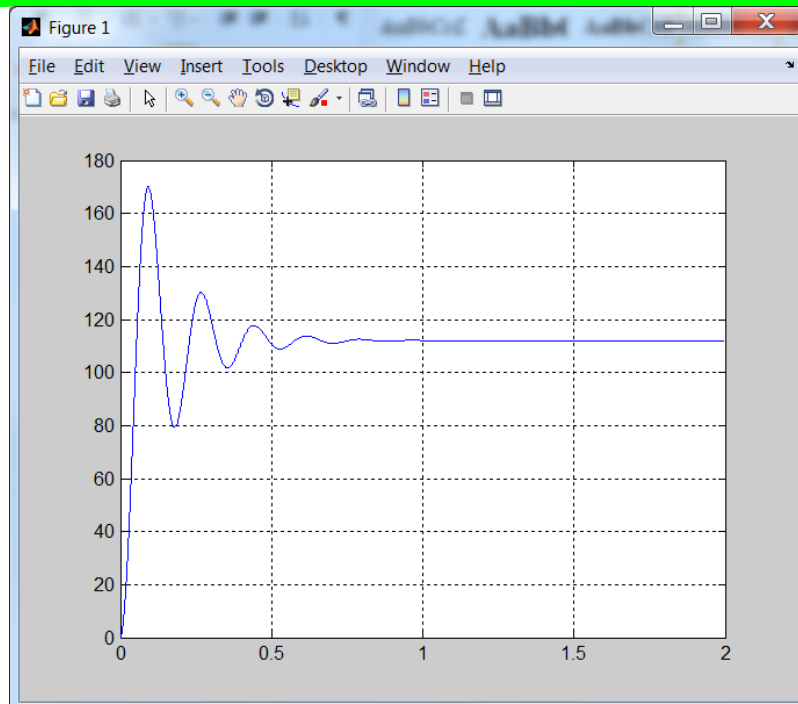

Problem 6

A three-phase short circuited induction AC motor is described by the following data:

$$J_m = J_{eff} = 0.005 \text{ kg} \cdot \text{m}^2, V_p = 220 \text{ V}, p = 2, f_s = 50 \text{ Hz}, R_s = 2 \, \Omega, R_r = 2.5 \, \Omega, \\ L_s = 0.025 \text{ H}, \text{ and } L_r = 0.015 \text{ H}.$$

The load on the rotor is a friction torque given as: $M_L = M_{fr} \cdot \tanh\left(\frac{\omega_m}{\omega_{fr}}\right)$, where $M_{fr} = 3 \text{ N} \cdot \text{m}$

and $\omega_{fr} = 20 \frac{\text{rad}}{\text{s}}$.

Initially the rotor has no rotation and is at rest. Simulate the system for a period of 1 seconds.

Solution as the motor torque, M_m , in Newton-meter vs. time in seconds.

